

Lect 19

Verilog HDL

CS221: Digital Design

Dr. A. Sahu
Dept of Comp. Sc. & Engg.
Indian Institute of Technology Guwahati

9/9/2018

Outline

- HDL Programming : Verilog HDL
- HDL Rules
- HDL Module and Examples
- HDL levels : Data flow, Structural and Behavioral, UDP
- Testing and Simulation


9/9/2018

What is Verilog

- Hardware Description Language (HDL)
- Developed in 1984
- Standard: IEEE 1364, Dec 1995

9/9/2018

Application Areas of Verilog

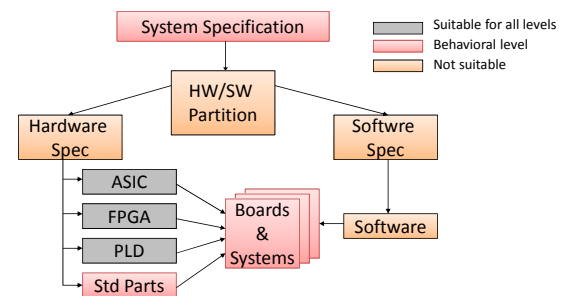

9/9/2018

HDL, Area of Application


- Design Entry
- Logic Simulation
- Functional Verification
- Digital Circuit Synthesis
- Timing Verification
- Fault Simulation
- Documentation

09/09/2018

5


Basic Limitation of Verilog

Description of digital systems only

 

9/9/2018


Abstraction Levels in Verilog

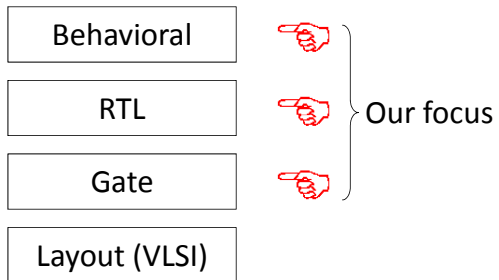


9/9/2018

Main Language Concepts (i)

- Concurrency

 



- Structure

 

9/9/2018

Main Language Concepts (ii)

- Procedural Statements
- Time

  


9/9/

Lets Start with an Example of Verilog HDL module

9/9/2018

Module

 

Everything you write in Verilog must be inside a module
exception: compiler directives


9/9/2018

Module

```
module my_module(out1, ..., inN);
    output out1, ..., outM;
    input in1, ..., inN;
    .. // declarations
    .. // description of f (maybe
    .. // sequential)
endmodule
```

Everything you write in Verilog must be inside a module
exception: compiler directives

Example: Half Adder

 

```
module half_adder(S,C,A,B);
output S, C;
input A, B;


wire S, C, A, B;

assign S = A ^ B;
assign C = A & B;

endmodule
```

9/9/2018

 Example: Half Adder (Data Flow Model: using Boolean Equations)



```
module half_adder(S,C,A,B);
output S, C;
input A, B;

wire S, C, A, B;

assign S = A ^ B;
assign C = A & B;

endmodule
```


```
assign S = A ^ B;
assign C = A & B;
```

```
assign C = A & B;
assign S = A ^ B;
```

Same

9/9/2018

Example: Half Adder, 2nd Implementation

 

```
module half_adder(S,C,A,B);
output S, C;
input A, B;


wire S, C, A, B;

xor (S, A, B);
and (C, A, B);

endmodule
```

9/9/2018

 Example: Half Adder, 2nd Implementation Using Structural/gate primitive inter connection



```
module half_adder(S,C,A,B);
output S, C;
input A, B;

wire S, C, A, B;

xor (S, A, B);
and (C, A, B);

endmodule
```

```
xor (S, A, B);
and (C, A, B);
```

```
and (C, A, B);
xor (S, A, B);
```

Same

9/9/2018

Verilog HDL Languages

9/9/2018

User Identifiers

- Formed from {[A-Z], [a-z], [0-9], _, \$}
- Can't begin with \$ or [0-9]
 - myidentifier
 - m_y_identifier
 - 3my_identifier
 - \$my_identifier
 - _myidentifier\$
- Case sensitivity : myid ≠ Myid

9/9/2018

Comments : same as C++ Style

- `// The rest of the line is a comment`
- `/* Multiple line
comment */`
- `/* Nesting /* comments */ do NOT
work */`

9/9/2018

Verilog Value Set

- **0** represents low logic level or false condition
- **1** represents high logic level or true condition
- **X** represents unknown logic level
- **Z** represents high impedance logic level == > open circuit

9/9/2018

Truth Tables (Updated..)

AND	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	x	x	X
Z	0	x	x	x

XOR	0	1	X	Z
0	0	1	X	X
1	1	0	X	X
X	X	x	x	X
Z	x	x	x	x

OR	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

NOT	0	1	X	Z
OUT	1	0	X	X

Sorry: There were two mistakes in this Slide, now corrected

9/9/2018

Numbers in Verilog (i)

`<size>'<radix> <value>`

No of bits

Binary → b or B
Octal → o or O
Decimal → d or D
Hexa → h or H

Consecutive chars
0-f, x, z

Examples:

–8'h ax = 1010 xxxx

–12'o 3zx7 = 011 zzz xxx 111

9/9/2018

Numbers in Verilog (ii)

- You can insert “_” for readability
 - 12'b 000_111_010_100
 - 12'b 000111010100
 - 12'o 07_24

} Represent the same number
- Bit extension
 - MS bit = 0, x or z ⇒ extend this
 - 4'b x1 = 4'b xx_x1
 - MS bit = 1 ⇒ zero extension
 - 4'b 1x = 4'b 00_1x

9/9/2018

Numbers in Verilog (iii)

- If *size* is omitted it
 - is inferred from the *value* or
 - takes the simulation specific number of bits or
 - takes the machine specific number of bits
- If *radix* is omitted too .. **decimal is assumed**
 - 15 = <size>d 15


9/9/2018

Nets (i)


- Can be thought as hardware wires driven by logic
- Equal z when unconnected
- Various types of nets
 - wire
 - wand (wired-AND)
 - wor (wired-OR)
 - tri (tri-state)
- In following examples: Y is evaluated, **automatically**, every time A or B changes

9/9/2018

Nets (ii)

 
 
```
wire Y; // declaration
assign Y = A & B;
```



```
wand Y; // declaration
assign Y = A;
assign Y = B;
```



```
tri Y; // declaration
assign Y = (dr) ? A : z;
```

		A
Y		0 1
0	0	0
B	1	0 1
		A
Y		0 1
0	0	1
B	1	1 1

9/9/2018

Registers

- Variables that store values
- Do not represent real hardware
- *But real hardware can be implemented with registers*
- Only one type: reg


```
reg A, C; // declaration
// assignments are always done inside a
// procedure
A = 1;
C = A; // C gets the logical value 1
A = 0; // C is still 1
C = 0; // C is now 0
```
- Register values are updated explicitly!!

9/9/2018

Vectors

- Represent buses

```
wire [3:0] busA;
reg [1:4] busB;
reg [1:0] busC;
```

- Left number is MS bit

- Slice management

```
busC = busA[2:1];
```

```
busC[1] = busA[2];
busC[0] = busA[1];
```

- Vector assignment (**by position!!**)

```
busB = busA;
```

```
busB[1] = busA[3];
busB[2] = busA[2];
busB[3] = busA[1];
busB[4] = busA[0];
```

9/9/2018

Integer & Real Data Types

- Declaration

```
integer i, k;
real r;
```

- Use as registers (inside procedures)

```
i = 1; // Asgmts occur in procedure
r = 2.9;
k = r; // k is rounded to 3
```

- Integers are not initialized!!
- Reals are initialized to 0.0

9/9/2018

Time Data Type

- Special data type for simulation time measuring
- Declaration

```
time my_time;
```

- Use inside procedure

```
my_time = $time;
// get current sim time
```

- Simulation runs at simulation time, not real time

9/9/2018

Strings

- Implemented with regs:

```
reg [8*13:1] string_val; // can hold up to 13 chars
string_val = "Hello Verilog";
string_val = "hello"; // MS Bytes are filled with 0
string_val = "I am overflowed"; // "I " is truncated
```

- Escaped chars:

```
- \n    newline    \t    tab
- %%    %          \\    \
- \"    "          \"    \"
```

9/9/2018

Logical Operators

- `&&` → logical AND
- `||` → logical OR
- `!` → logical NOT
- Operands evaluated to ONE bit value: 0, 1 or x
- Result is ONE bit value: 0, 1 or x

```
A = 6;      A && B → 1 && 0 → 0
B = 0;      A || !B → 1 || 1 → 1
C = x;      C || B → x || 0 → x
```

but C && B = 0

9/9/2018

Bitwise Operators (i)

- `&` → bitwise AND
- `|` → bitwise OR
- `~` → bitwise NOT
- `^` → bitwise XOR
- `~^` or `^~` → bitwise XNOR
- Operation on bit by bit basis
- Two operand needed

9/9/2018


Reduction Operators

- `&` → AND
- `|` → OR
- `^` → XOR
- `~&` → NAND
- `~|` → NOR
- `~^` or `^~` → XNOR
- One multi-bit operand → One single-bit result**

```
a = 4'b1001;
c = |a; // c = 1|0|0|1 = 1
```

9/9/2018

Example: using primitive gates

 

```
module Simple_Circuit (A,B,C,D,E);
    output D,E;
    input A,B,C;
    wire w1;
    and G1 (w1,A,B);
    not G2 (E,C);
    or G3 (D,w1,E);
endmodule
```

09/09/2018

35


Delays

- Propagation delay
 - Specified in terms of time units
 - Specified by the symbol #
- and #10 G1 (w1, A,B)
- Association of time unit and time scale is made with the compiler directive `'timescale`
 - Specified before the declaration of a module
 - `'timescale 1 ns/100ps` indicates unit of measurement for time delay

09/09/2018

36

Test Bench

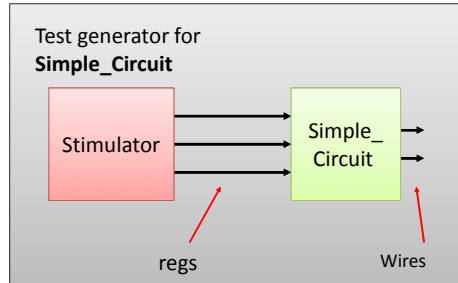

09/09/2018

37


Test Bench for Simple_Circuit

```

module t_Simple_Circuit_delay;
wire D,E;
reg A,B,C;
Simple_Circuit_delay M1 (A,B,C,D,E); //Instantiation of M1
initial
begin
A= 1'b0; B=1'b0; C=1'b0;
#100 A=1'b1; B=1'b1; C=1'b1;
end
Initial #200 $finish;
endmodule

```

Example With Delay

 



```

module Simple_Circuit_with_delay
(A,B,C,D,E);
output D,E;
input A,B,C;
wire w1;
and #(30) G1 (w1,A,B);
not #(10) G2 (E,C);
or #(20) G3 (D,w1,E);
endmodule

```

Time (ns)	A	B	C	Ew1D
Initial	0	0	0	1 0 1
initial	1	1	1	1 0 1
10	1	1	1	0 0 1
20	1	1	1	0 0 1
30	1	1	1	0 1 0
40	1	1	1	0 1 0
50	1	1	1	0 1 1

Example

  

09/09/2018

40