

**Lect 14****Binary Multiplier****CS221: Digital Design**

Dr. A. Sahu  
Dept of Comp. Sc. & Engg.  
Indian Institute of Technology Guwahati

1

**Outline**

- Array Binary Multiplier
- Sequential Multiplier
- High Radix Multiplier
- Booth Multiplier
- Programmable logic Device (PLD)
  - PLA, PAL, ROM, GAL, CPLD, CLB
  - Software .....HDLs

2


**Delay of Adder**

- Ripple Carry Adder (RCA) =  $N * T_c = \alpha N$
- Manchester RCA =  $N * T_m = \alpha N$
- Carry Skip Adder  
Total Delay =  $p (N/m) T_s + (p-1) * (N/m) * m * T_c$   
 $T = N * (p/m * T_s + (p-1) T_c) = \alpha N$
- Carry Select Adder = Independent of Data  
Delay of select =  $T_s$   
 $T = (N/m - 1) T_s + m T_c$   
 $T = N * T_c / m + (m T_c - T_s) = \alpha N + c$
- CLA :  $\log_4 N$ , Area:  $O(2N)$


4

**Efficient  
Multiplier Design****Multiplication: paper - pencil method**


A	0	1	1				
B	1	0	1				
	0	1	1		0	0	0
	0	0	0	x		0	0
	0	1	1	x		0	0
AxB	0	1	1	1		0	1

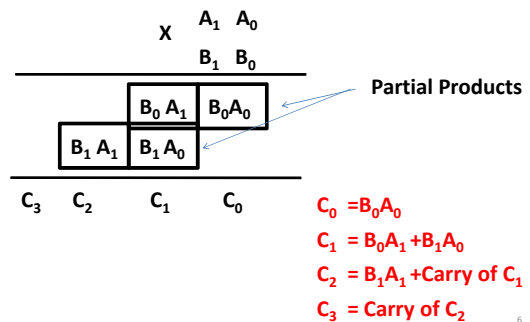**Binary Multiplier: 2 Bits**


### Binary Multiplier: 2 Bits

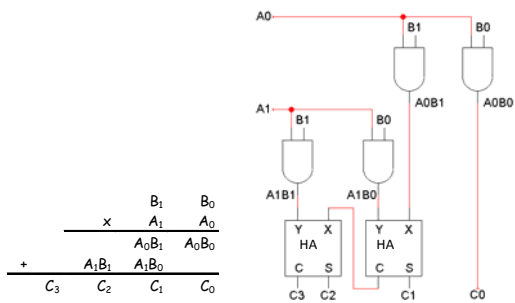

### Binary Multiplier: 4 Bits

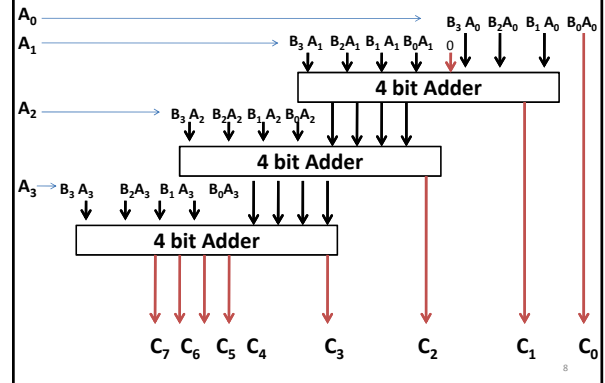

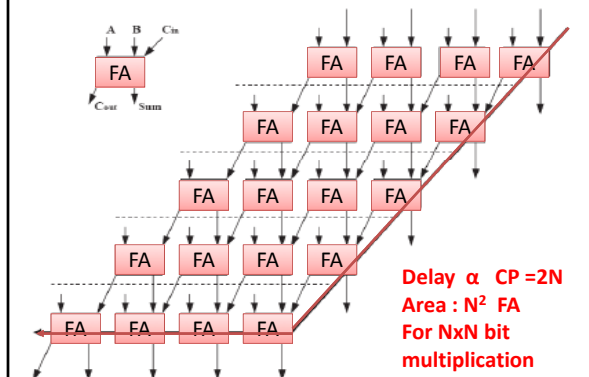
### Area & Delay (Critical Path): Multiplier



### Multiply: Shift & Add

- Decimal number :  $15 \times 20 = 300$ ,  $10 \times 20 + 5 \times 20 = 300$
- Binary number:  $1111 \times 10100$ 
  - $1000 \times 10100 + 100 \times 10100 + 10 \times 10100 + 1 \times 10100$
  - $\text{Sft3}(10100) + \text{sft2}(10100) + \text{sft1}(10100) + \text{sft0}(10100)$
  - $1111 \times 10000 + 1111 \times 100$
  - $\text{Sft5}(1111) + \text{sft2}(1111)$
- Multiplication of N bit number, N shift, N Add, if bit is zero don't add
- Special addition


### Shift add multiplier

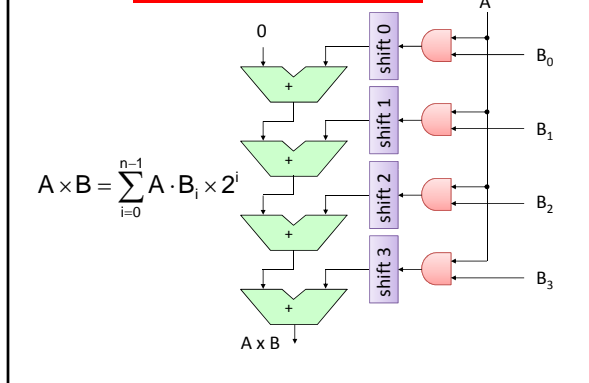
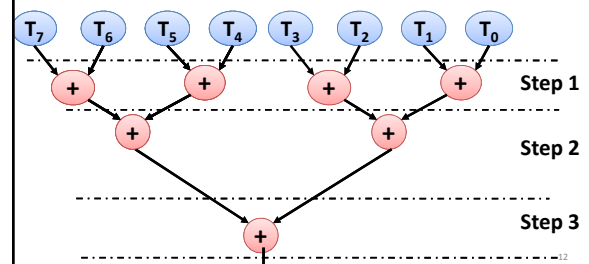
### Simple Speeding up

$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i = \sum_{i=0}^{n-1} T_i$$

$$= A \cdot B_0 \times 2^0 + A \cdot B_1 \times 2^1 + \dots + A \cdot B_{n-1} \times 2^{n-1}$$



### Simple Speeding up

$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i = \sum_{i=0}^{n-1} T_i$$

$$= A \cdot B_0 \times 2^0 + A \cdot B_1 \times 2^1 + \dots + A \cdot B_{n-1} \times 2^{n-1}$$

- **Assumption: Generate All the term in parallel**
- N Addition can be done in parallel in Log(N) steps using N/2 Adder.
- **Adder complexity is Linear O(N) using RCA**
  - Area : Number of Adder\*Area Per Adder = N/2 \* N
  - Delay : Delay per Adder\* Steps = N. lg N
- **Adder complexity CLA Log (N)**
  - Area : Number of Adder\*Area Per Adder = N/2 \* 2N
  - Delay : Delay per Adder\* Steps = lg N. lg N = (lg N)<sup>2</sup>

### Algorithm Serial Multiplication: D & C

- To multiply two n-digit integers:
  - Multiply **four** ½n-digit integers.
  - Add two ½n-digit integers, and shift to obtain result.

$$x = 2^{n/2} \cdot x_1 + x_0$$

$$y = 2^{n/2} \cdot y_1 + y_0$$

$$xy = (2^{n/2} \cdot x_1 + x_0)(2^{n/2} \cdot y_1 + y_0) = 2^n \cdot x_1 y_1 + 2^{n/2} \cdot (x_1 y_0 + x_0 y_1) + x_0 y_0$$

$$T(n) = \underbrace{4T(n/2)}_{\text{recursive calls}} + \underbrace{\Theta(n)}_{\text{add, shift}} \Rightarrow T(n) = \Theta(n^2)$$

### Improved: Karatsuba Multiplication

- To multiply two n-digit integers:
  - Add two ½n digit integers.
  - Multiply **three** ½n-digit integers. (Re use of Term)

$$x = 2^{n/2} \cdot x_1 + x_0$$

$$y = 2^{n/2} \cdot y_1 + y_0$$


$$xy = 2^n \cdot x_1 y_1 + 2^{n/2} \cdot (x_1 y_0 + x_0 y_1) + x_0 y_0$$

$$= 2^n \cdot x_1 y_1 + 2^{n/2} \cdot ((x_1 + x_0)(y_1 + y_0) - x_1 y_1 - x_0 y_0) + x_0 y_0$$

$$T(n) = \underbrace{3T(n/2)}_{\text{recursive calls}} + \underbrace{\Theta(n)}_{\text{add, shift}} \Rightarrow T(n) = \Theta(n^{\log_2 3}) = \Theta(n^{1.58})$$
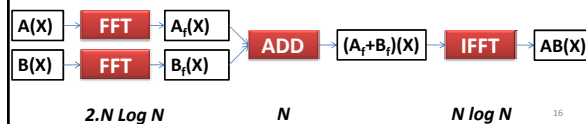
### N bit Multiplication: FFT Method

- Idea:  $1024 \cdot 16 = 2^{10} \cdot 2^4 = 2^{10+4} = 2^{14} = 16384$
- FFT based multiplication
  - N Bit binary numbers  $A(X) = A_{n-1}2^{n-1} + A_{n-2}2^{n-2} + \dots + A_0 \cdot 1$
  - Polynomial multiplication  $A(X) * B(X)$
  - $A(X) * B(X) = \text{IFFT}(\text{FFT}(A(X)) + \text{FFT}(B(X)))$
  - Complexity :  $2n \lg n + n + n \lg n = O(n \lg n)$




### Shift add multiplier (sequential)

$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i$$

step1: i=0; s=0 do { step2: s += A · B <sub>i</sub> × 2 <sup>i</sup> i ++ } while (i < n)	step1: i=0; s=0 do { step2: if (B <sub>i</sub> ) s += A A = 2xA i ++ } while (i < n)	step1: i=0; s=0 do { step2: if (B <sub>0</sub> ) s += A A = 2xA B = B/2; i ++ } while (i < n)
--	--	---

### Sequential shift add multiplier 1

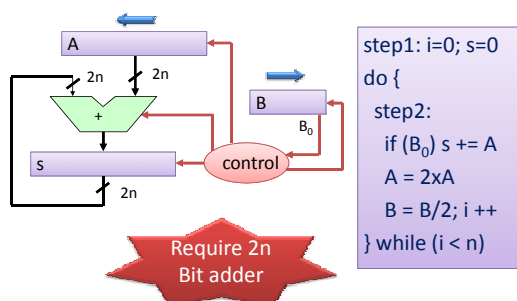


```


step1: i=0; s=0
do {
  step2:
  if (B0) s += A
  A = 2xA
  B = B/2; i ++
} while (i < n)

```

### Sequential shift add multiplier 2

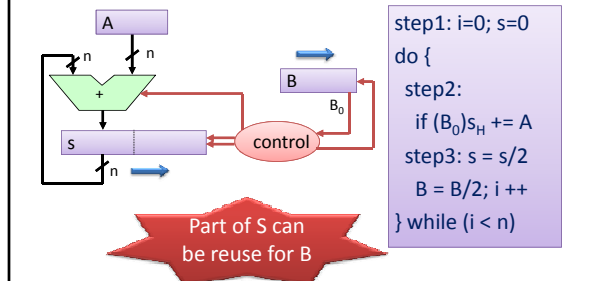


### Sequential shift add multiplier 3

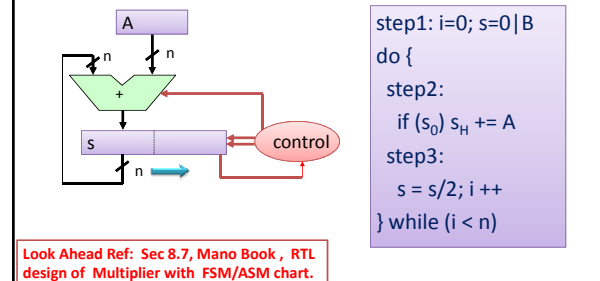


### Higher Radix Multiplication

21
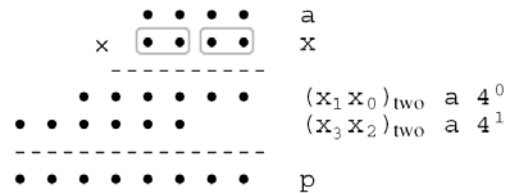
### Radix-4, or two-bit-at-a-time, multiplication in dot notation


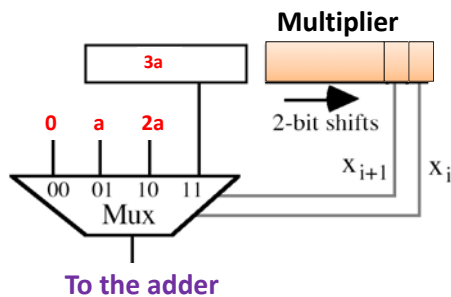
### Multiple generation part of a radix-4 multiplier with precomputation of $3a$



### Higher Radix Multiplication

- In radix-8, one must precompute  $3a, 5a, 7a$   
– Overhead becomes prohibitive and does not help

## Higher Radix Multiplication Booth Encoding

25

## Radix-2 Booth Recoding

$\begin{matrix} & j+1 & j & i \\ 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 1 & 0 & \text{Operand } x \\ (1) & -1 & 0 & 1 & 0 & 0 & -1 & 1 & 0 & -1 & 1 & -1 & 1 & 0 & 0 & 0 & -1 & 0 & \text{Recoded version } y \end{matrix}$

Justification

$$2^j + 2^{j-1} + \dots + 2^{i+1} + 2^i = 2^{i+1} - 2^j$$

## Radix-2 Booth Recoding

$x_i$	$x_{i-1}$	$y_i$	Explanation
0	0	0	No string of 1s in sight
0	1	1	End of string of 1s in x
1	0	-1	Beginning of string of 1s in x
1	1	0	Continuation of string of 1s in x

$\begin{matrix} 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 1 & 0 & 1 & 1 & 1 & 0 & \text{Operand } x \\ (1) & -1 & 0 & 1 & 0 & 0 & -1 & 1 & 1 & 1 & 1 & 0 & 0 & -1 & 0 & \text{Recoded version } y \end{matrix}$

$$y_i = -x_i + x_{i-1}$$

## Radix-2 Booth Multiplier Basic Step

