

Lect 15

Programmable Logic

CS221: Digital Design

Dr. A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline


- Programmable Logic
- PAL, PLA,
- Memory
 - ROM, PROM, EPROM, EEPROM
 - SRAM : Memory Cell
- CPLD, CLB, FPGA
- FPGA/ASIC Design Flow
- HDL Programming : Verilog HDL

Programmable Logic Devices

Programmable Via Control :


Adder/Subtractor

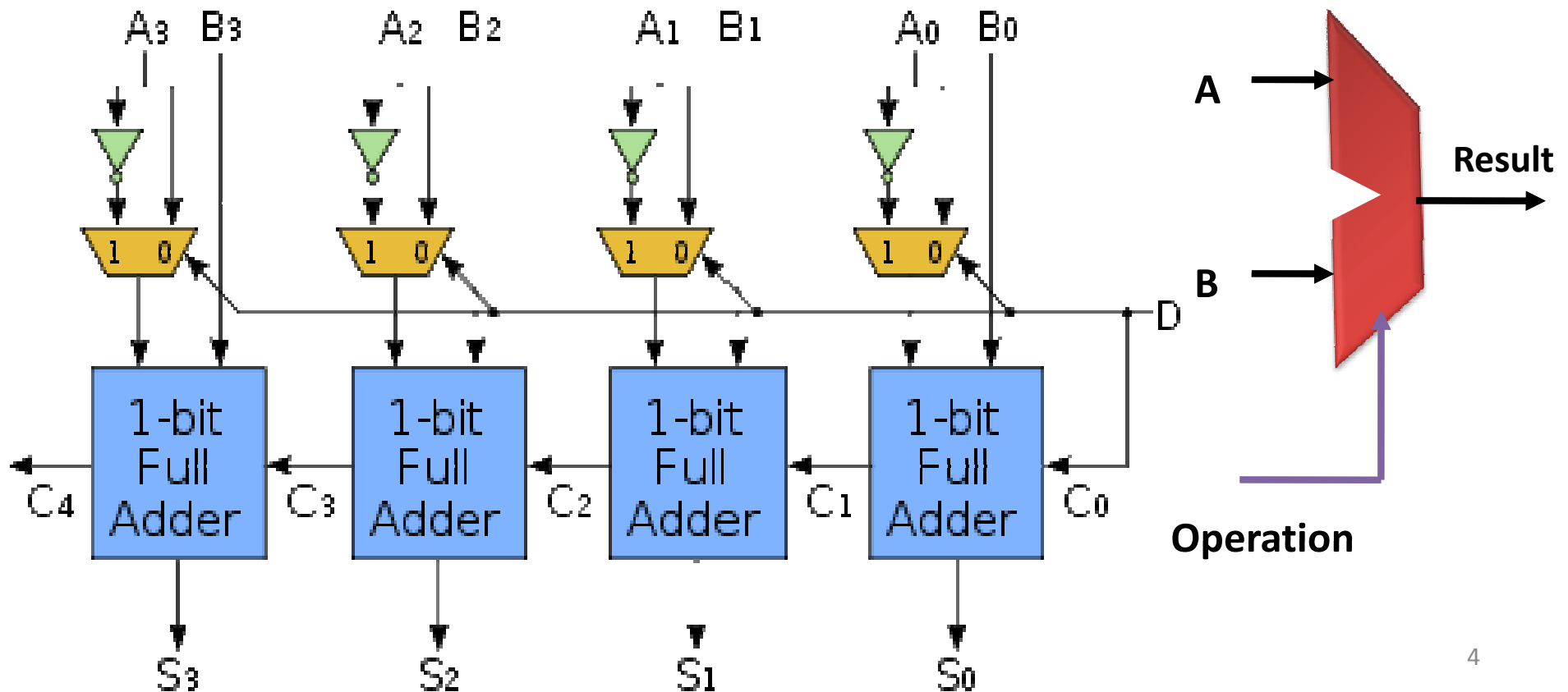- $C = B - A = B + (-A) = B + (A^b + 1)$, A^b is complement of A
- D is control bit: D=0/1 operation is add/sub



Programmable Via Select: ALU

 - Arithmetic and Logic Unit
- Add/Sub/OR/AND/Shift...




Control: What to do ?

if Control=0	$R = A + B$
if Control=1	$R = A - B$
if Control=2	$R = \text{NOT } A$
if Control=3	$R = A \text{ AND } B$
if Control=4	$R = A \text{ OR } B$
if Control=5	$R = A \text{ XOR } B$
if Control=6	$R = (A < B) ? 0 : A$
if Control=7	$R = A \text{ SHFT } B$

Programmable Logic Devices

Programmable Logic Organization

 - Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
- "Personalized" by making or breaking connections among the gates



Programmable Array Block Diagram for Sum of Products Form

Basic Programmable Logic Organizations

- Depending on which of the AND/OR logic arrays is programmable, we have three basic organizations

ORGANIZATION	AND ARRAY	OR ARRAY
PAL	PROG.	FIXED
PROM	FIXED	PROG.
PLA	PROG.	PROG.

PLA Logic Implementation

Key to Success: **Shared** Product Terms

Example: Equations

$$F_0 = A + B' C'$$

$$F_1 = A C' + A B$$

$$F_2 = B' C' + A B$$

$$F_3 = B' C + A$$

Personality Matrix

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
A B	1	1	-	0	①	①	0
B' C	-	0	1	0	0	0	1
A C'	1	-	0	0	1	0	0
B' C'	-	0	0	①	0	①	0
A	1	-	-	①	0	0	①

Reuse of terms

Input Side:

1 = asserted in term

0 = negated in term

- = does not participate


Output Side:

1 = term connected to output

0 = no connection to output


PLA Logic Implementation

Example Continued - Unprogrammed device

 

PLA Logic Implementation


Example Continued - Programmed part

 

PLA Logic Implementation

Alternative representation

Un-programmed device

 

Short-hand notation so we don't have to
draw all the wires!

X at junction indicates a connection


PLA Logic Implementation

Notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

Programmed device

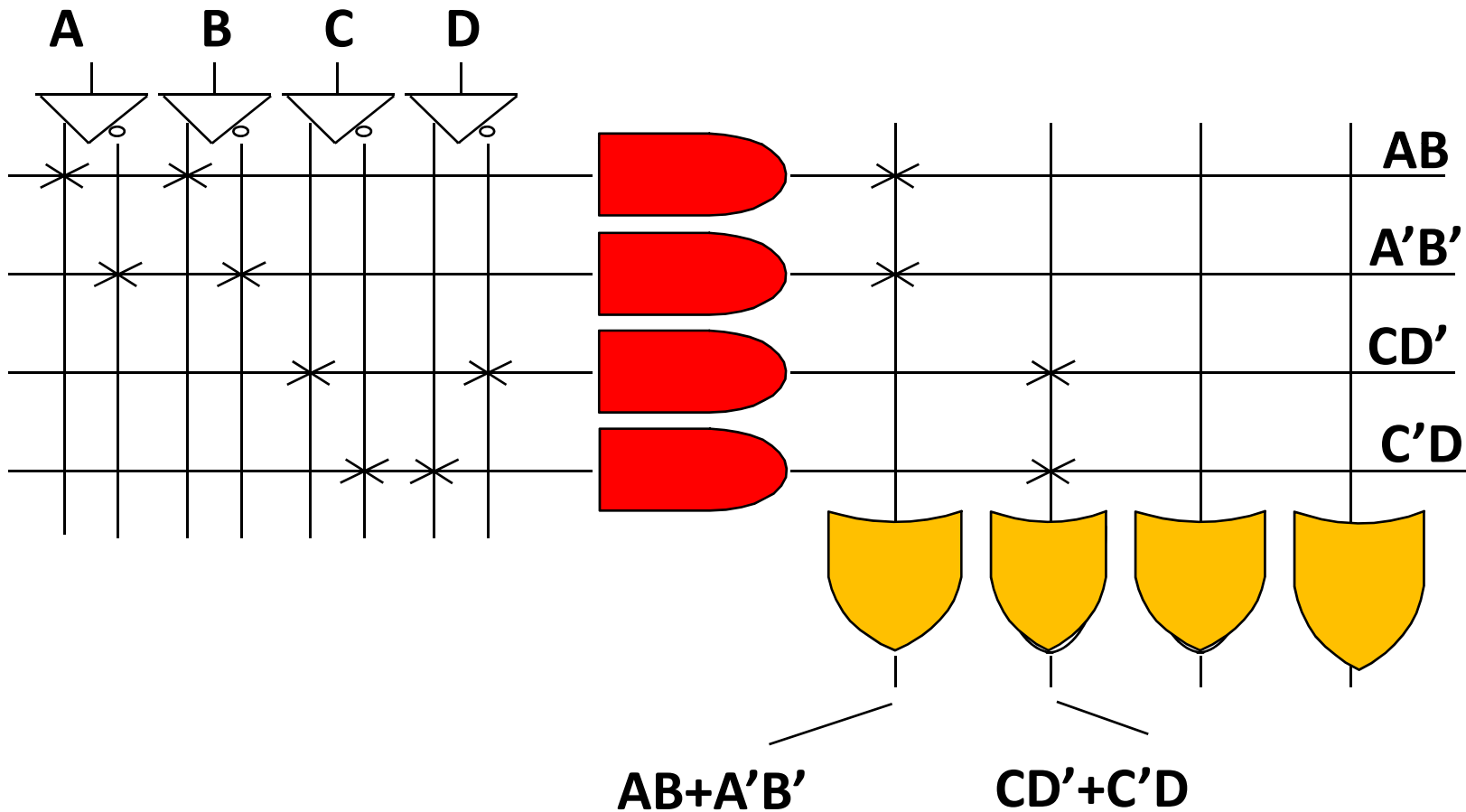


PLA Logic Implementation

Multiple functions of A, B, C : List of all product terms





Design Example
 
$$\begin{aligned}F1 &= A B C \\F2 &= A + B + C \\F3 &= (A B C)' \\F4 &= (A + B + C)' \\F5 &= A \oplus B \oplus C \\F6 &= (A \oplus B \oplus C)'\end{aligned}$$




PLA Logic Implementation

Another Example: Magnitude Comparator

 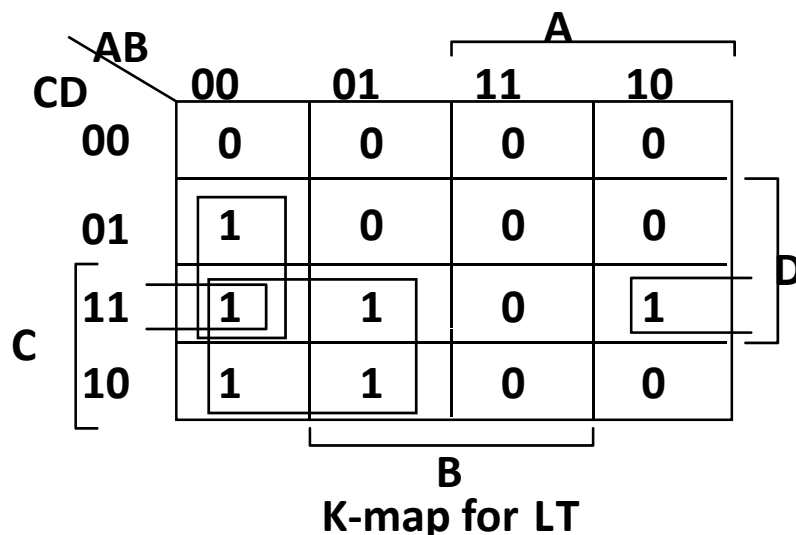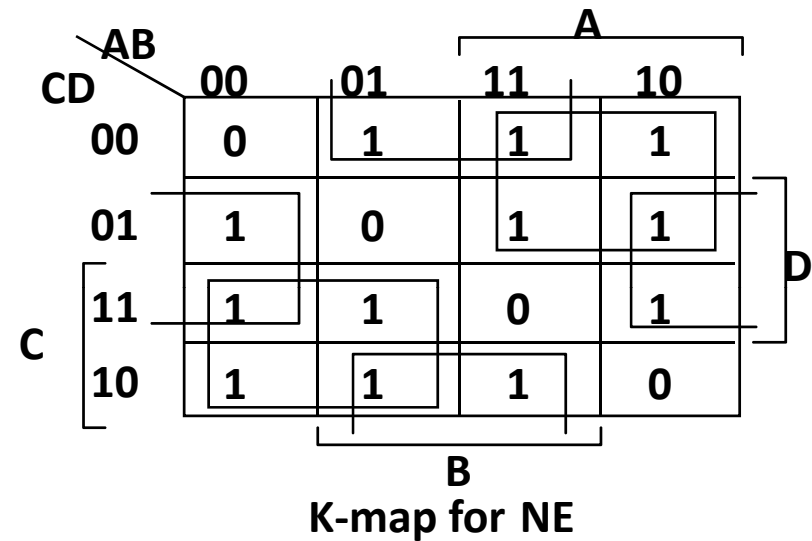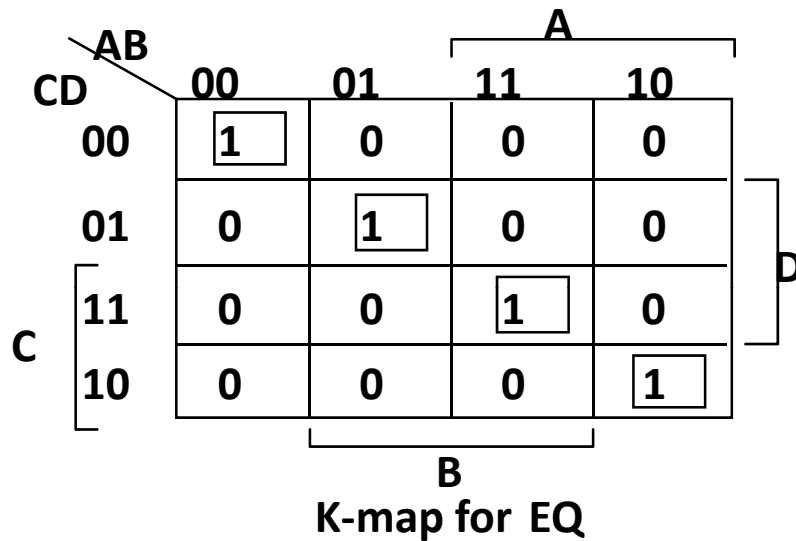


PLA Logic Imp: Magnitude Comparator

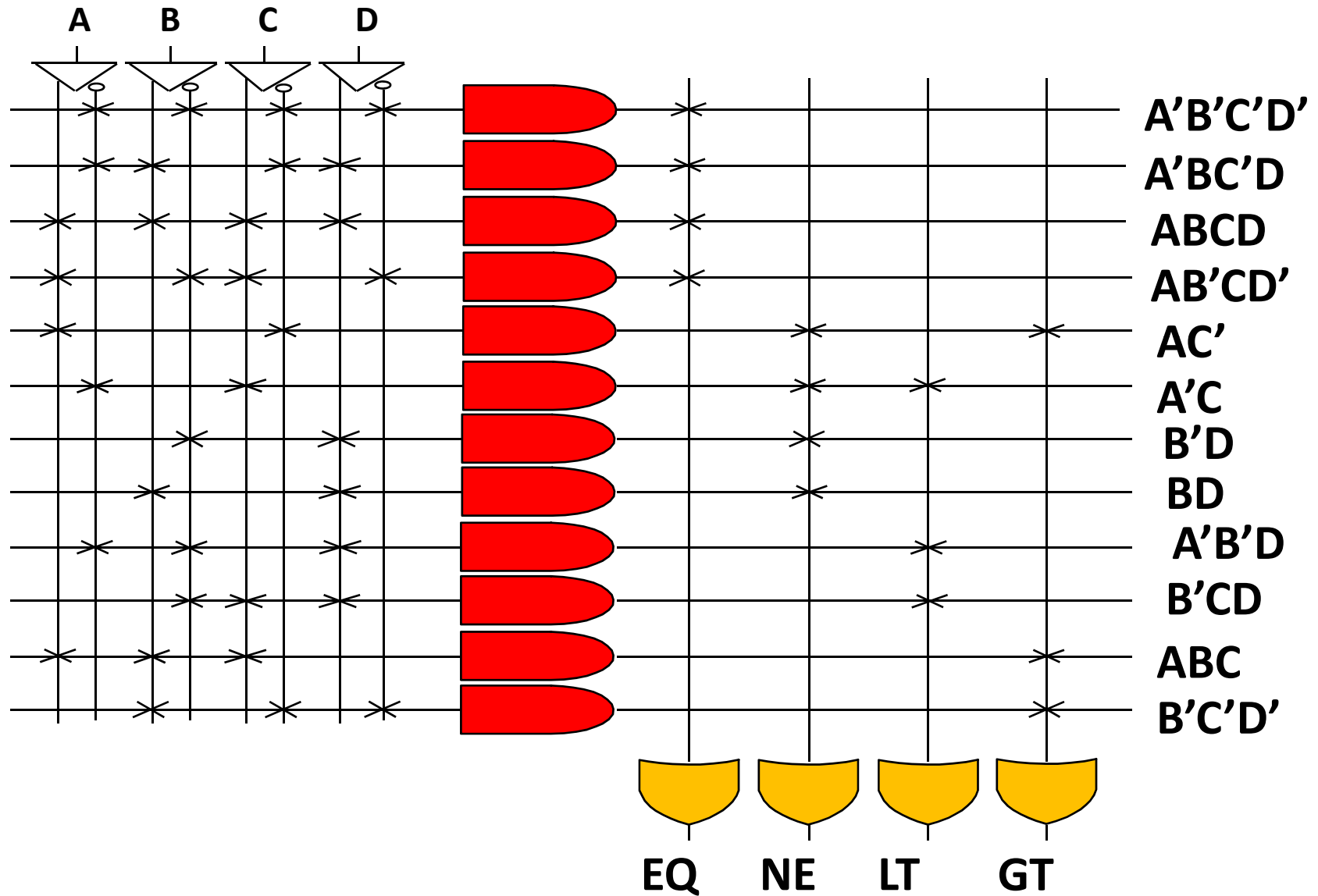

PALs and PLAs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 **PAL concept — implemented by Monolithic Memories
AND array is programmable, OR array is fixed at fabrication**



A given column of the OR array has access to only a subset of the possible product terms

PLA concept — Both AND and OR arrays are programmable

PALs and PLAs


- Of the two organizations the PLA is the most flexible
 - One PLA can implement a huge range of logic functions
 - BUT many pins; large package, higher cost
- PALs are more restricted / you trade number of OR terms vs number of outputs
 - Many device variations needed
 - **Each device is cheaper than a PLA**

Read-Only Memory

ROM


ROM

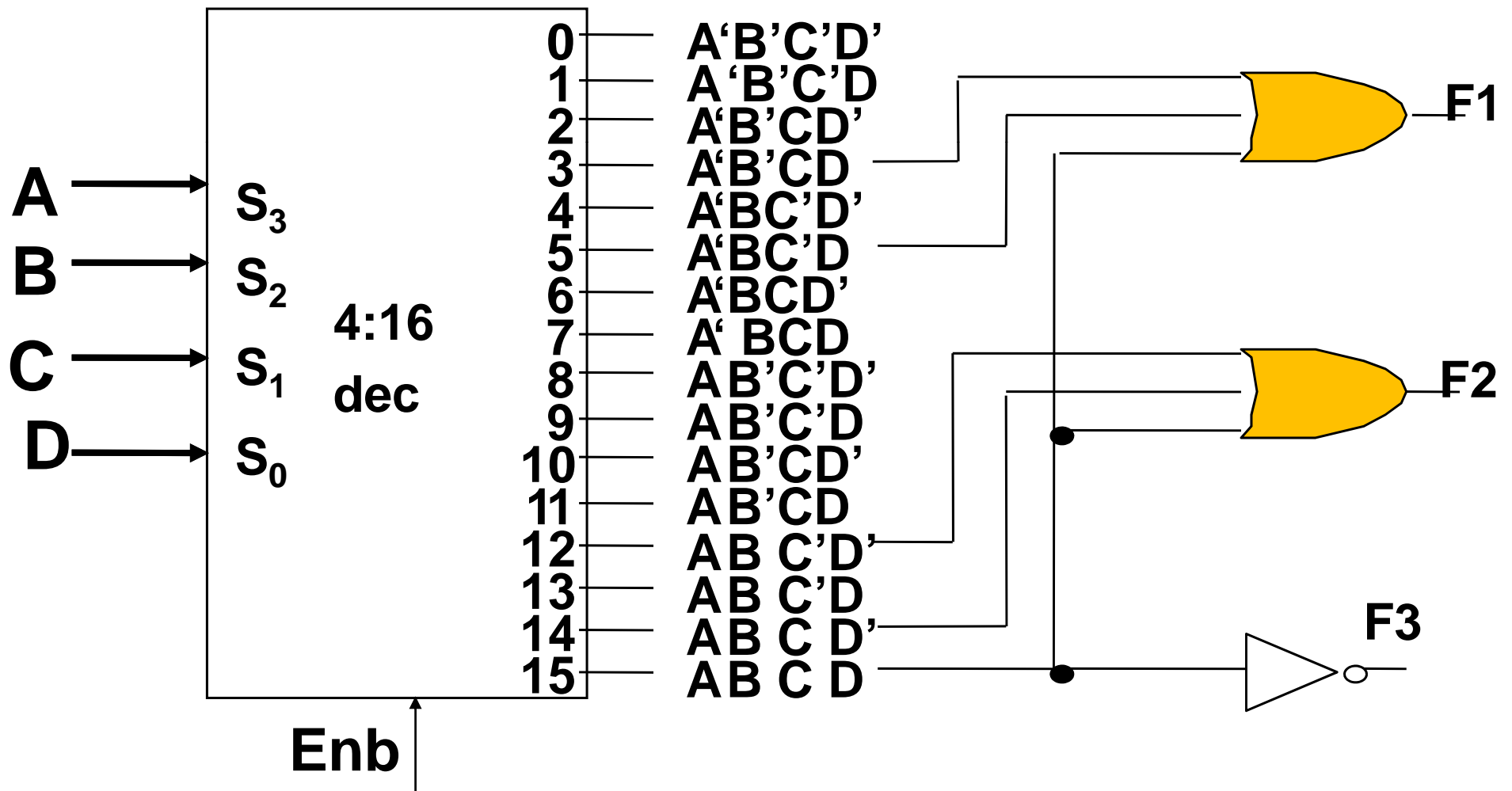- **Decoder** : Produces minterms
- **Ors** : Produce SOP's




ROM


- A decoder
- A set of programmable OR's

 


ROM vs. PLA/PAL

 

(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

General Logic Implementation

- Given a $2^k \times n$ ROM, we can implement ANY combinational circuit with at most k inputs and at most n outputs.
- Why?
 - k -to- 2^k decoder will generate all 2^k possible minterms
 - Each of the OR gates must implement a $\Sigma m()$
 - Each $\Sigma m()$ can be programmed


Example

- Find a ROM-based circuit implementation for:
 - $f(a,b,c) = a'b' + abc$
 - $g(a,b,c) = a'b'c' + ab + bc$
 - $h(a,b,c) = a'b' + c$
- Solution:
 - Express $f()$, $g()$, and $h()$ in $\sum m()$ format (use truth tables)
 - Program the ROM based on the 3 $\sum m()$'s

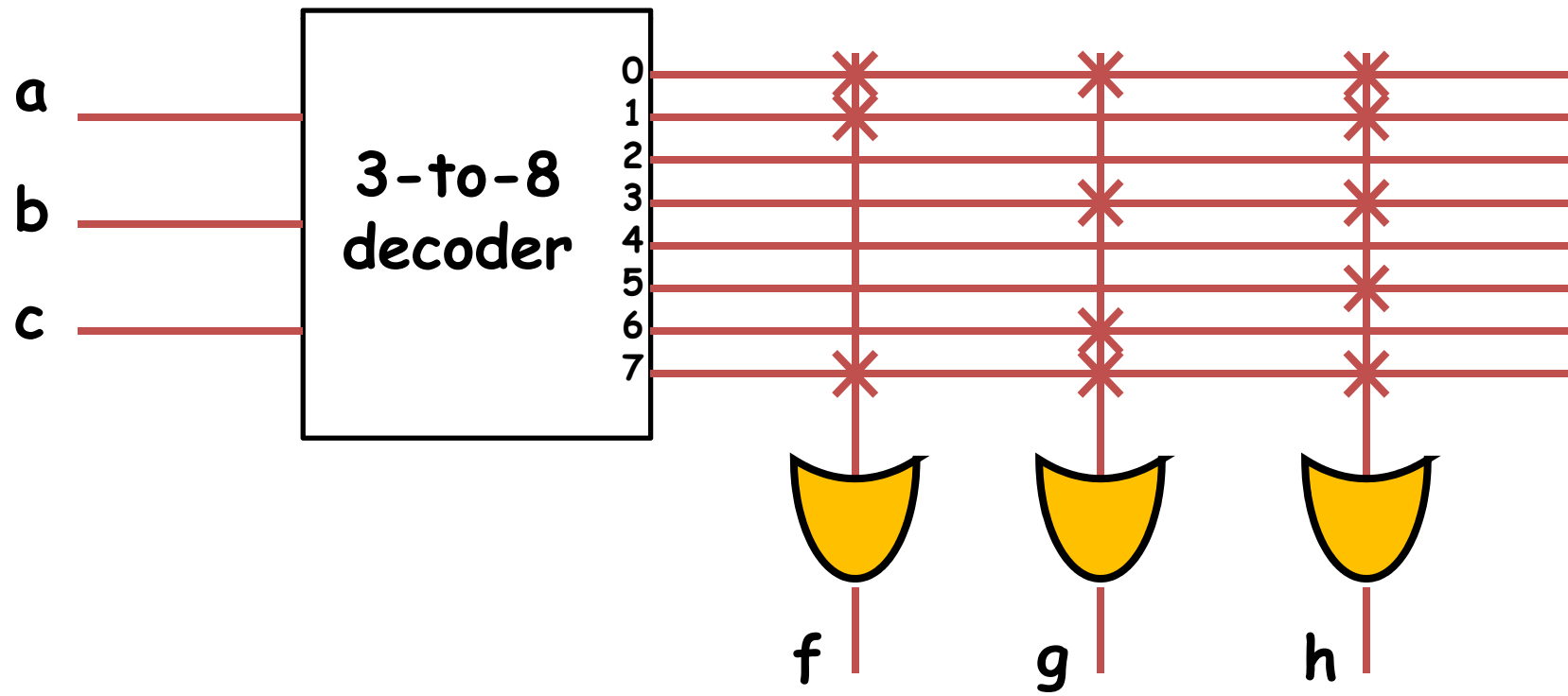Example

- There are 3 inputs and 3 outputs, thus we need a 8x3 ROM block.

$$f = \sum m(0, 1, 7), \quad g = \sum m(0, 3, 6, 7), \quad h = \sum m(0, 1, 3, 5, 7)$$



ROM as a Memory


- Read Only Memories (ROM) or Programmable Read Only Memories (PROM) have:
 - N input lines,
 - M output lines, and
 - 2^N decoded minterms.
- Can be viewed as a memory with the inputs as addresses of data (output values),
 - hence ROM or PROM names!

Memories

- Volatile: Random Access Memory (RAM)
 - SRAM "static"
 - DRAM "dynamic"
- Non-Volatile: Read Only Memory (ROM):
 - Mask ROM "mask programmable"
 - EPROM "electrically programmable"
 - EEPROM "electrically erasable electrically programmable"
 - FLASH memory - similar to EEPROM with programmer integrated on chip

ROM as Memory

 - **Read Example:** For input $(A_2, A_1, A_0) = 011$, output is $(F_0, F_1, F_2, F_3) = 0010$.
- What are functions F_3, F_2, F_1 and F_0 in terms of (A_2, A_1, A_0) ?




$$A[2:0] = A_2A_1A_0 \quad F[3:0] = F_3F_2F_1F_0$$


Design by ROM: Example

- BCD to 7 Segment Display Controller


A B C D	a	b	c	d	e	f	g
0 0 0 0	1	1	1	1	1	1	0
0 0 0 1	0	1	1	0	0	0	0
0 0 1 0	1	1	0	1	1	0	1
0 0 1 1	1	1	1	1	0	0	1
0 1 0 0	0	1	1	0	0	1	1
0 1 0 1	1	0	1	1	0	1	1
0 1 1 0	1	0	1	1	1	1	1
0 1 1 1	1	1	1	0	0	0	0
1 0 0 0	1	1	1	1	1	1	1
1 0 0 1	1	1	1	0	0	1	1
1 0 1 0	X	X	X	X	X	X	X
1 0 1 1	X	X	X	X	X	X	X
1 1 0 0	X	X	X	X	X	X	X
1 1 0 1	X	X	X	X	X	X	X
1 1 1 0	X	X	X	X	X	X	X
0 1 1 1	X	X	X	X	X	X	X

 


Memory Unit

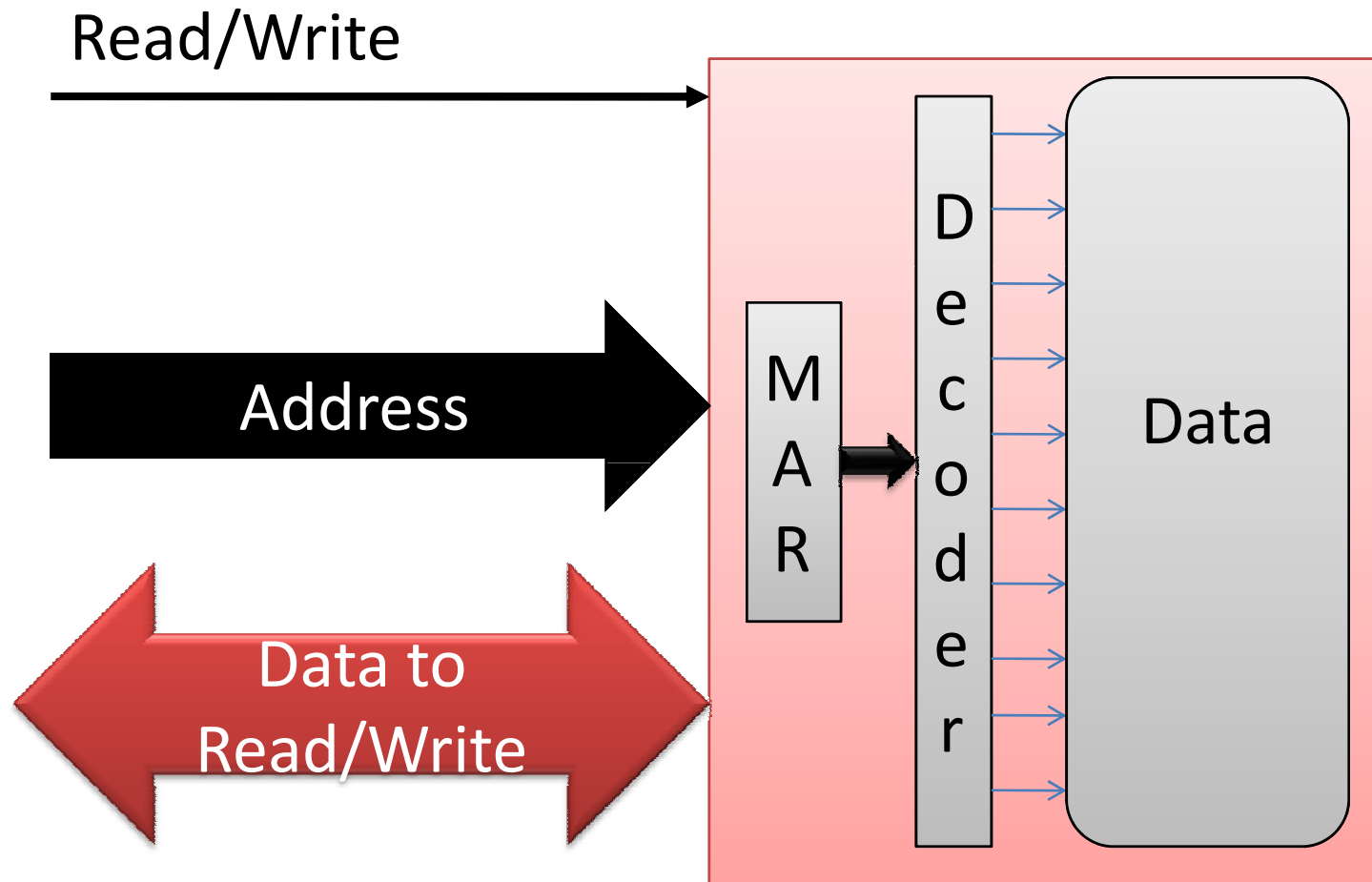

Memory Unit

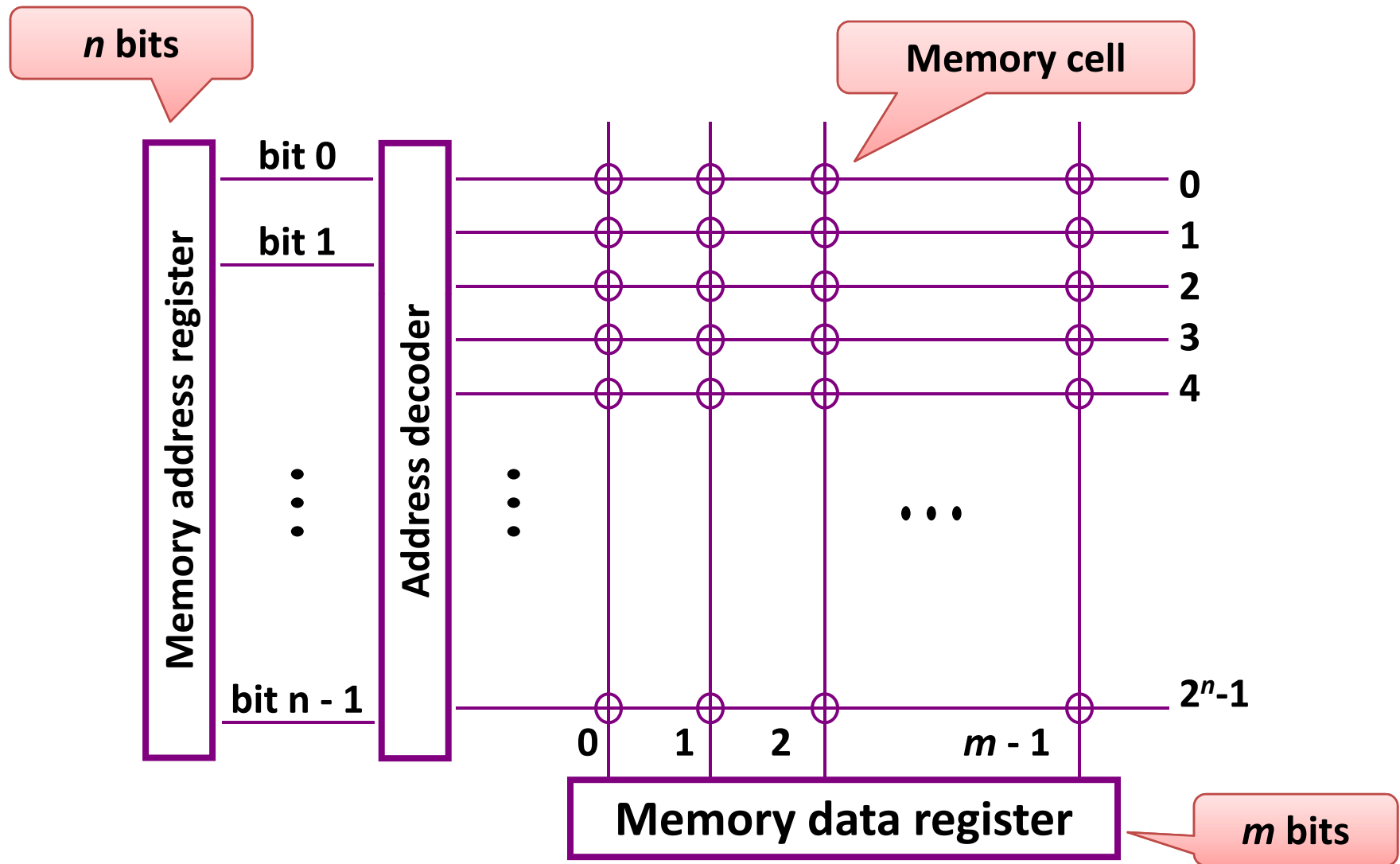

Memory Cell

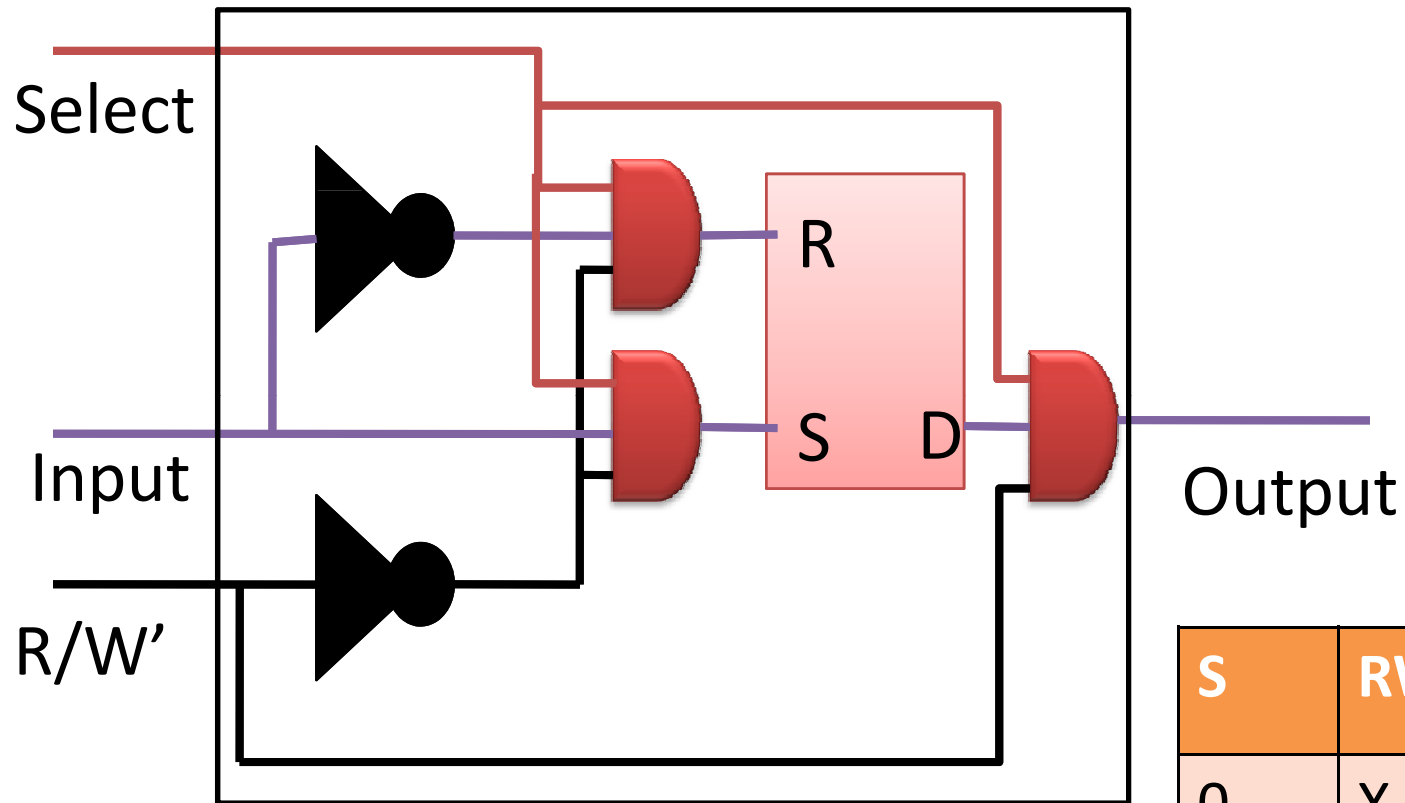

S	RW'	D	O/p
0	X	X	0
1	1	X	D
1	0	In	0

Memory

