

Lect 16

Programmable Logic and Hardware Programming (Verilog HDL)

CS221: Digital Design

Dr. A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

Outline

- Programmable Logic
- PAL, PLA,
- Memory
 - ROM, PROM, EPROM, EEPROM
 - SRAM : Memory Cell
- CPLD, CLB, FPGA
- FPGA/ASIC Design Flow
- HDL Programming : Verilog HDL

Programmable Logic Organization

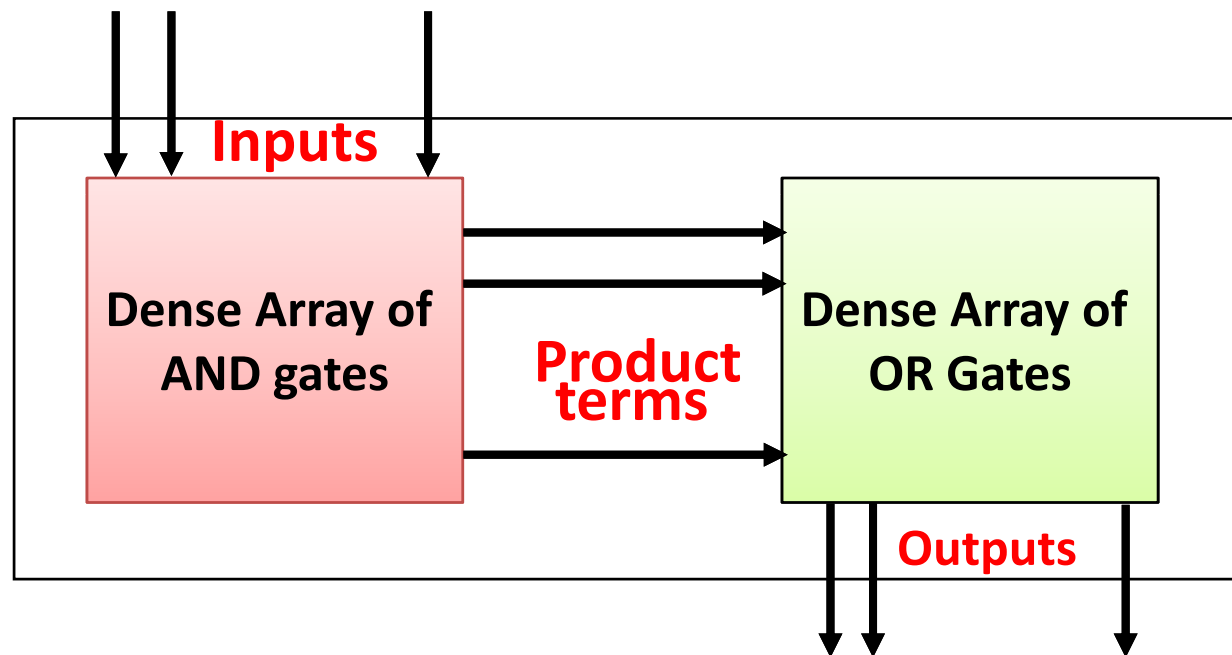- Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
- "Personalized" by making or breaking connections among the gates




9/2/2018 *Programmable Array Block Diagram for Sum of Products Form*

1. PLA Logic Implementation

Alternative representation

Un-programmed device

 


Short-hand notation so we don't have to
draw all the wires!

X at junction indicates a connection

 2. PALs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

**PAL concept — implemented by Monolithic Memories
AND array is programmable, OR array is fixed at fabrication**




A given column of the OR array has access to only a subset of the possible product terms

9/2/2018


PLA concept — Both AND and OR arrays are programmable

 3. ROM as Memory

- **Read Example:** For input $(A_2, A_1, A_0) = 011$, output is $(F_0, F_1, F_2, F_3) = 0010$.
- What are functions F_3, F_2, F_1 and F_0 in terms of (A_2, A_1, A_0) ?




4. SRAM: Memory Cell

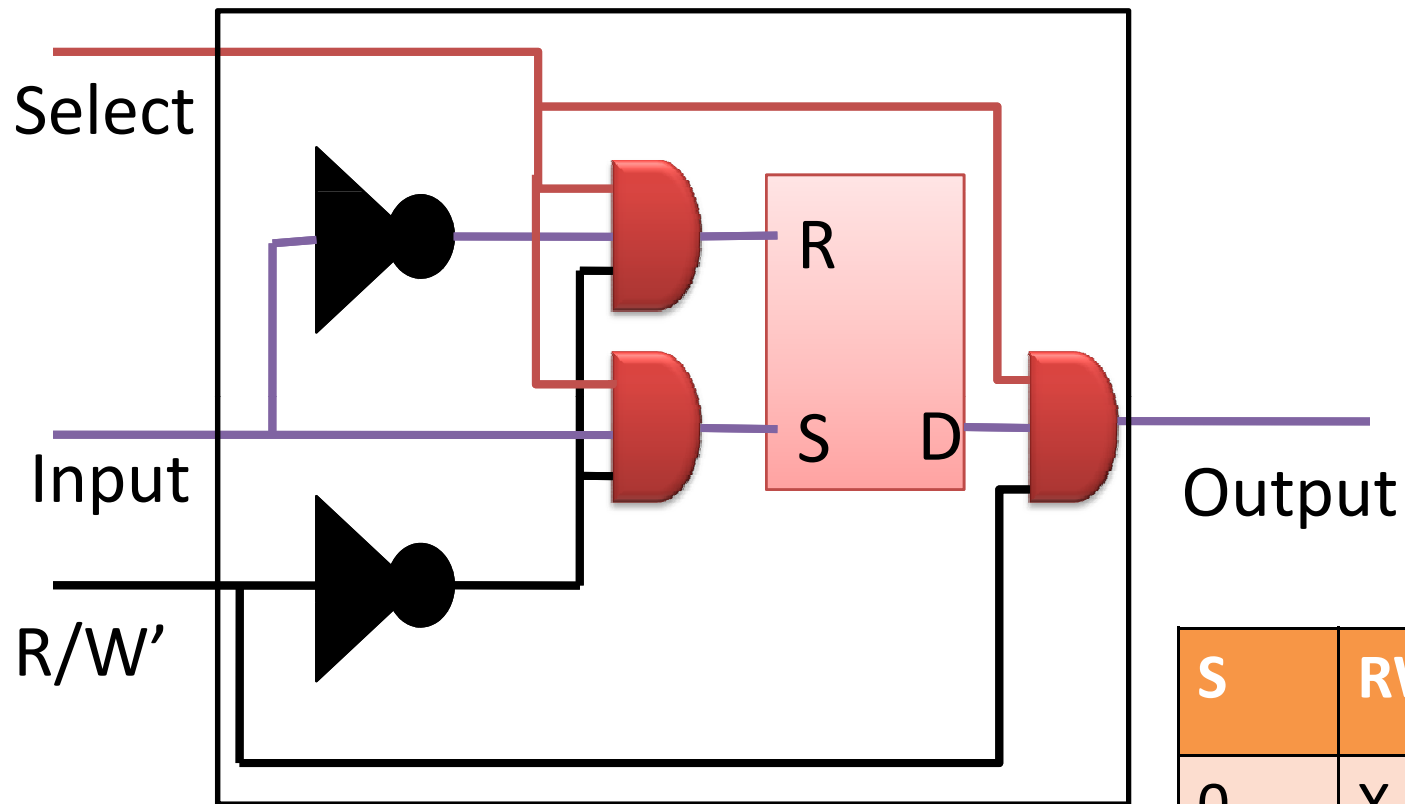

S	RW'	D	O/p
0	X	X	0
1	1	X	D
1	0	In	0

4. SRAM : Memory

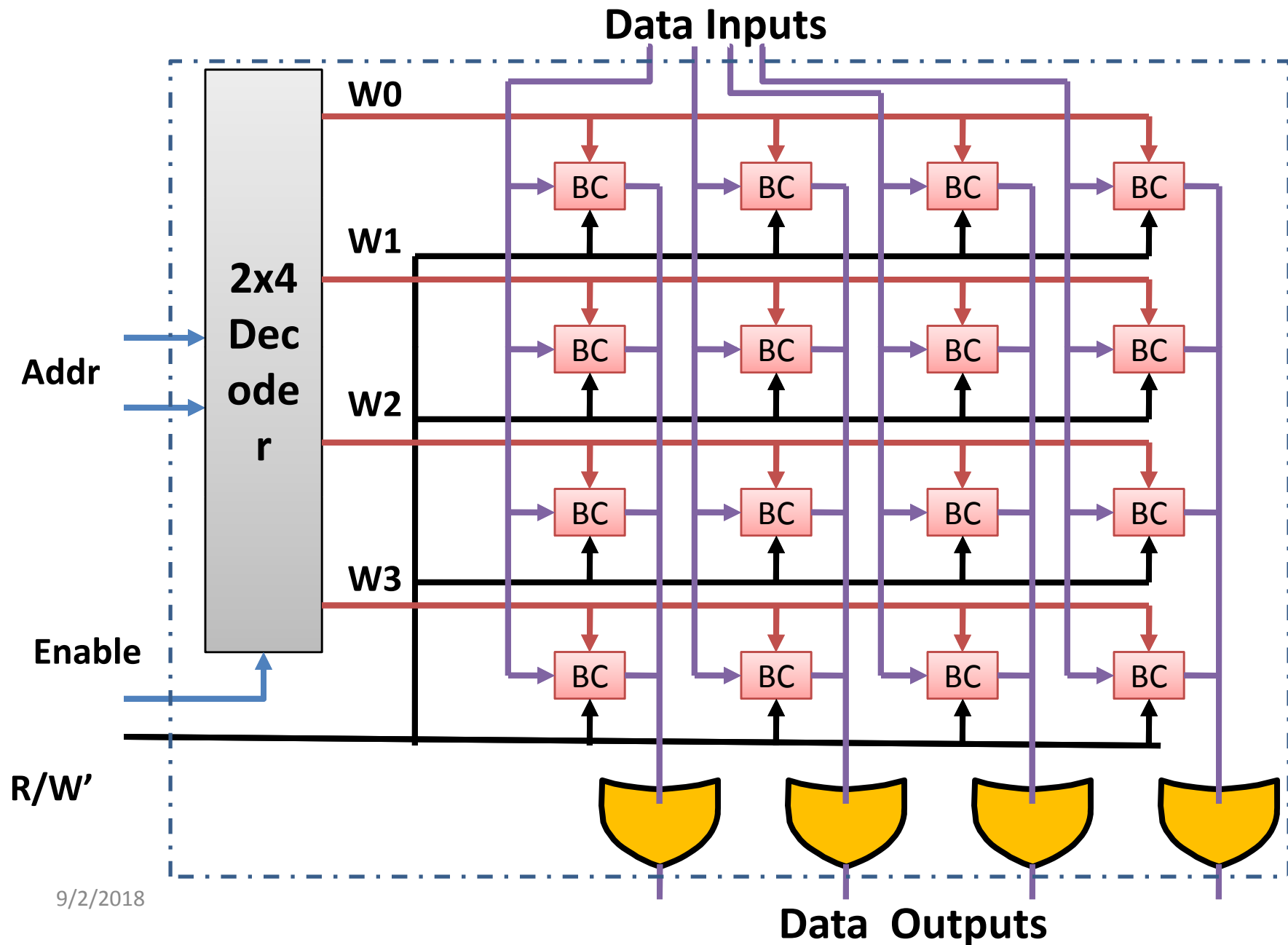


Advanced Programmable Logic Devices

SPLD , CPLD and FPGA

- Simple Programmable logic device
 - Single AND Level
 - Flip-Flops and feedbacks
- Complex Programmable logic device
 - Several PLDs Stacked together


SPLD - CPLD

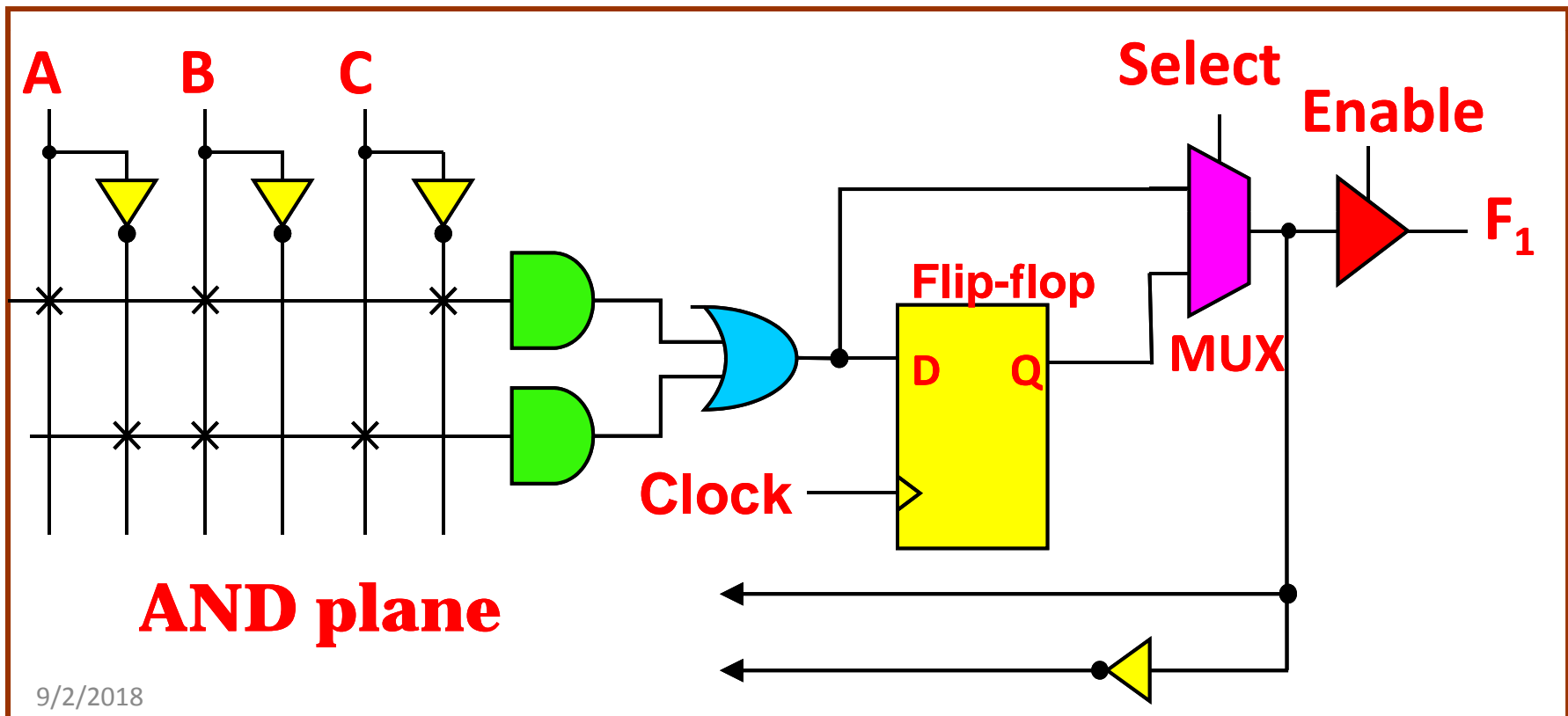- Simple Programmable logic device
 - Single AND Level
 - Flip-Flops and feedbacks



SPLD - CPLD

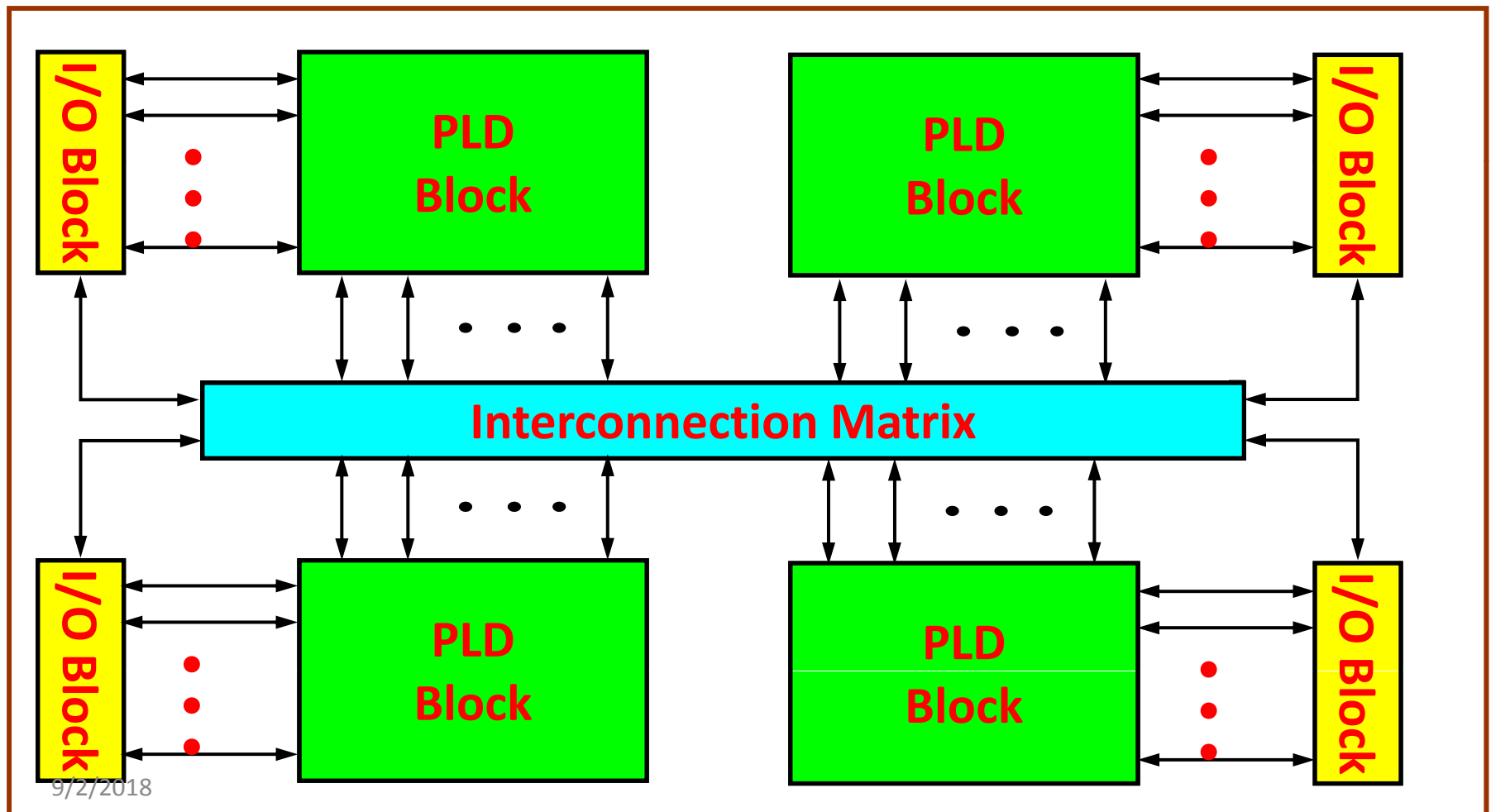- Complex Programmable logic device
 - Several PLDs Stacked together



FPGA

Field Programmable Gate Arrays (FPGAs)


- FPGAs have much more logic than CPLDs
 - 2K to >10M equivalent gates
 - Requires different architecture
 - FPGAs can be RAM-based or Flash-based
 - RAM FPGAs must be programmed at power-on
 - External memory needed for programming data
 - May be dynamically reconfigured
 - Flash FPGAs store program data in non-volatile memory
 - Reprogramming is more difficult
 - Holds configuration when power is off

FPGA - Field Programmable Gate Array

- Programmable logic blocks (Logic Element “LE”) or CLB
 - Implement combinatorial and sequential logic. Based on LUT and DFF.
- Programmable I/O blocks
 - Configurable I/Os for external connections supports various voltages and tri-states.
- Programmable interconnect
 - Wires to connect inputs , outputs and logic blocks.
 - Clocks
 - short distance local connections
 - long distance connections across chip

FPGA - Field Programmable Gate Array

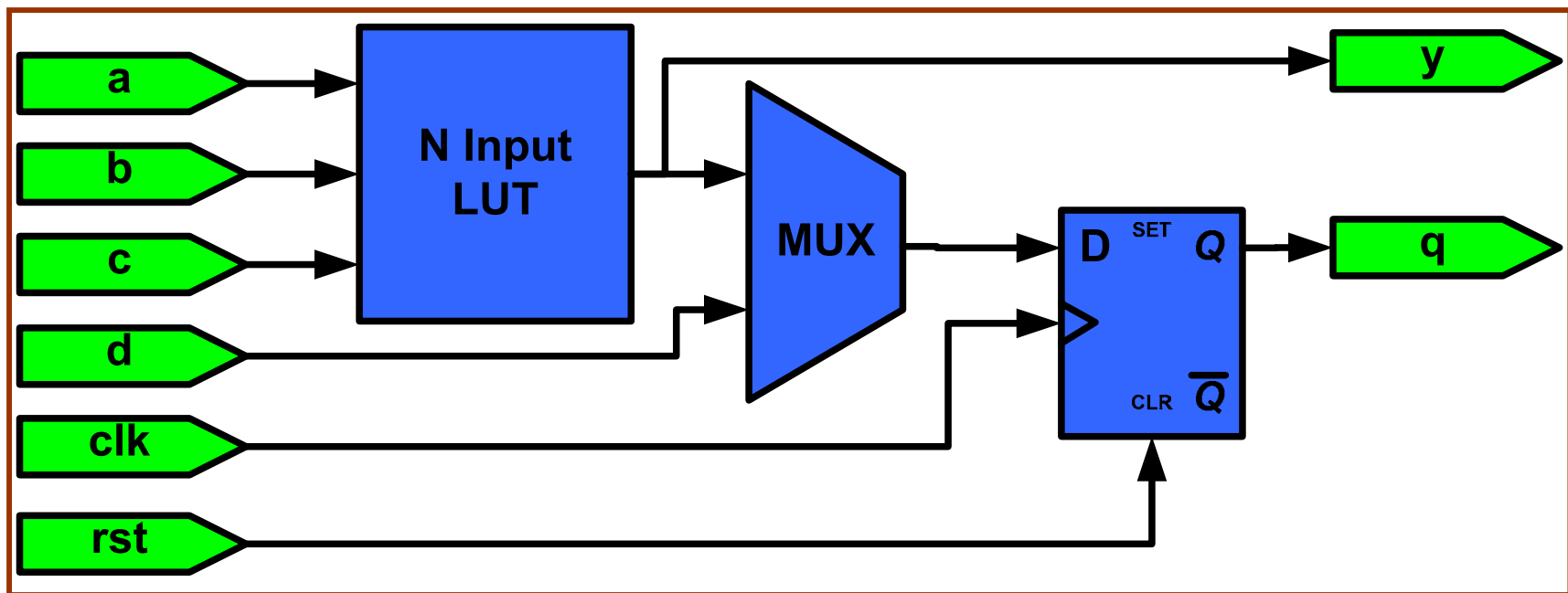
- Programmable logic blocks or CLB
 - (Logic Element “LE”)
 - Implement combinatorial and sequential logic.
Based on LUT and DFF.



Configuring LUT

- LUT is a RAM with data width of 1bit.
- The contents are programmed at power up


Required Function

 

Truth Table

a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Programmed LUT

 


FPGA - Field Programmable Gate Array



Logic block



Interconnection switches

 

Field-Programmable Gate Arrays structure

- **Logic blocks**

- To implement combinational and sequential logic

- **Interconnect**


- Wires to connect inputs and outputs to logic blocks

- **I/O blocks**



- Special logic blocks at periphery of device for external connections

- **Key questions:**

 
- How to make logic blocks programmable?
- How to connect the wires?



FPGA structure

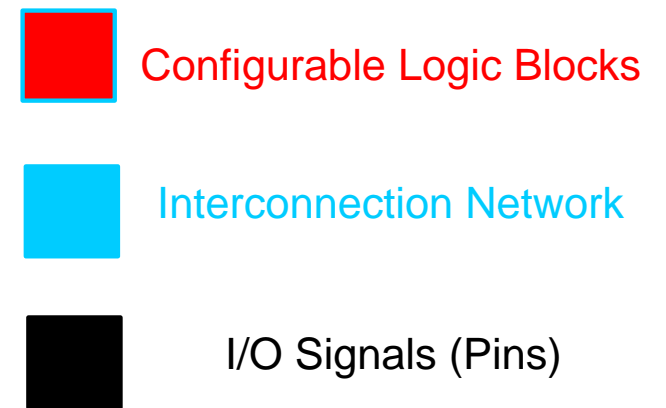 


Simplified CLB Structure

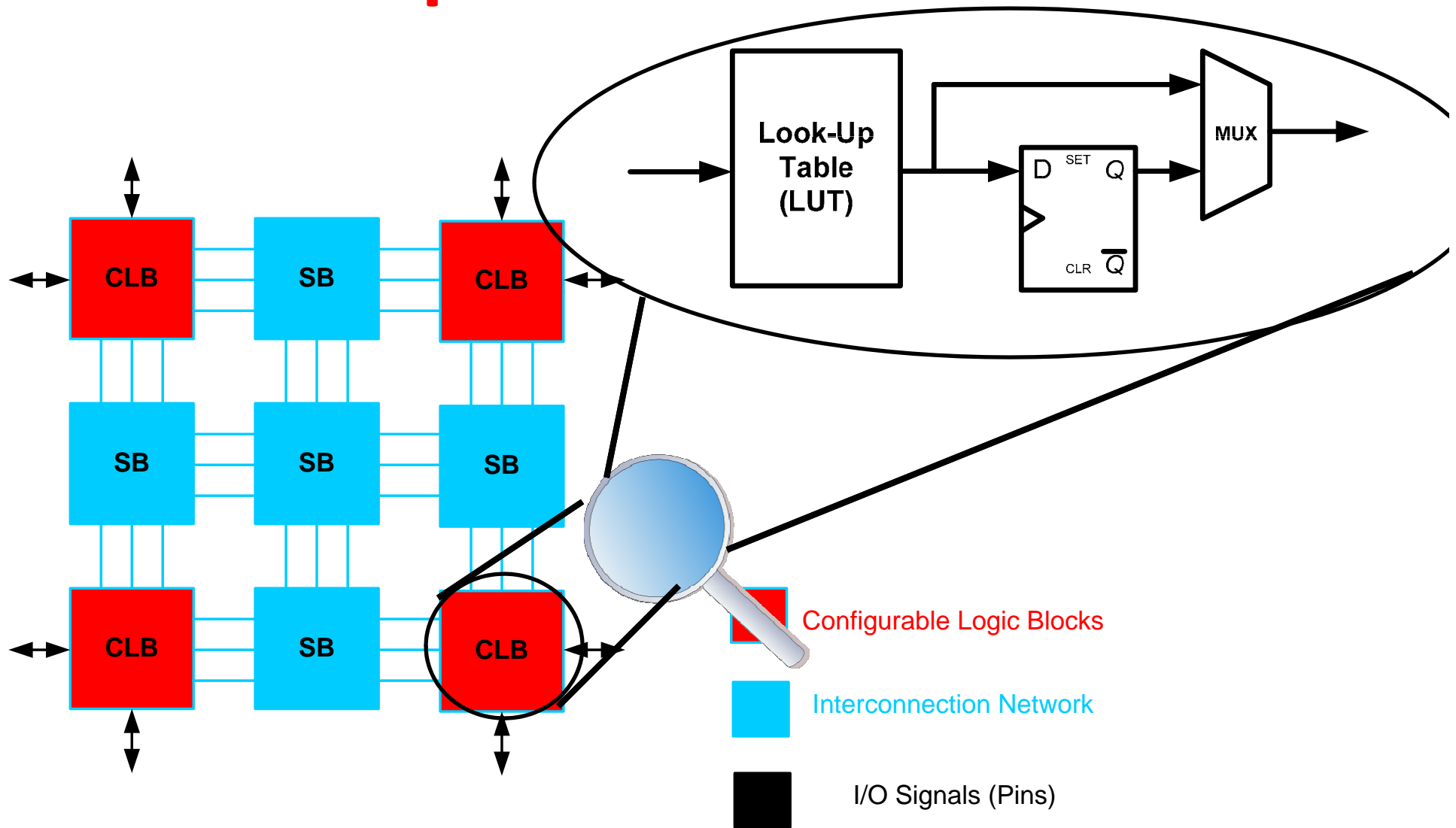


Example: 4-input AND gate


A	B	C	D	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

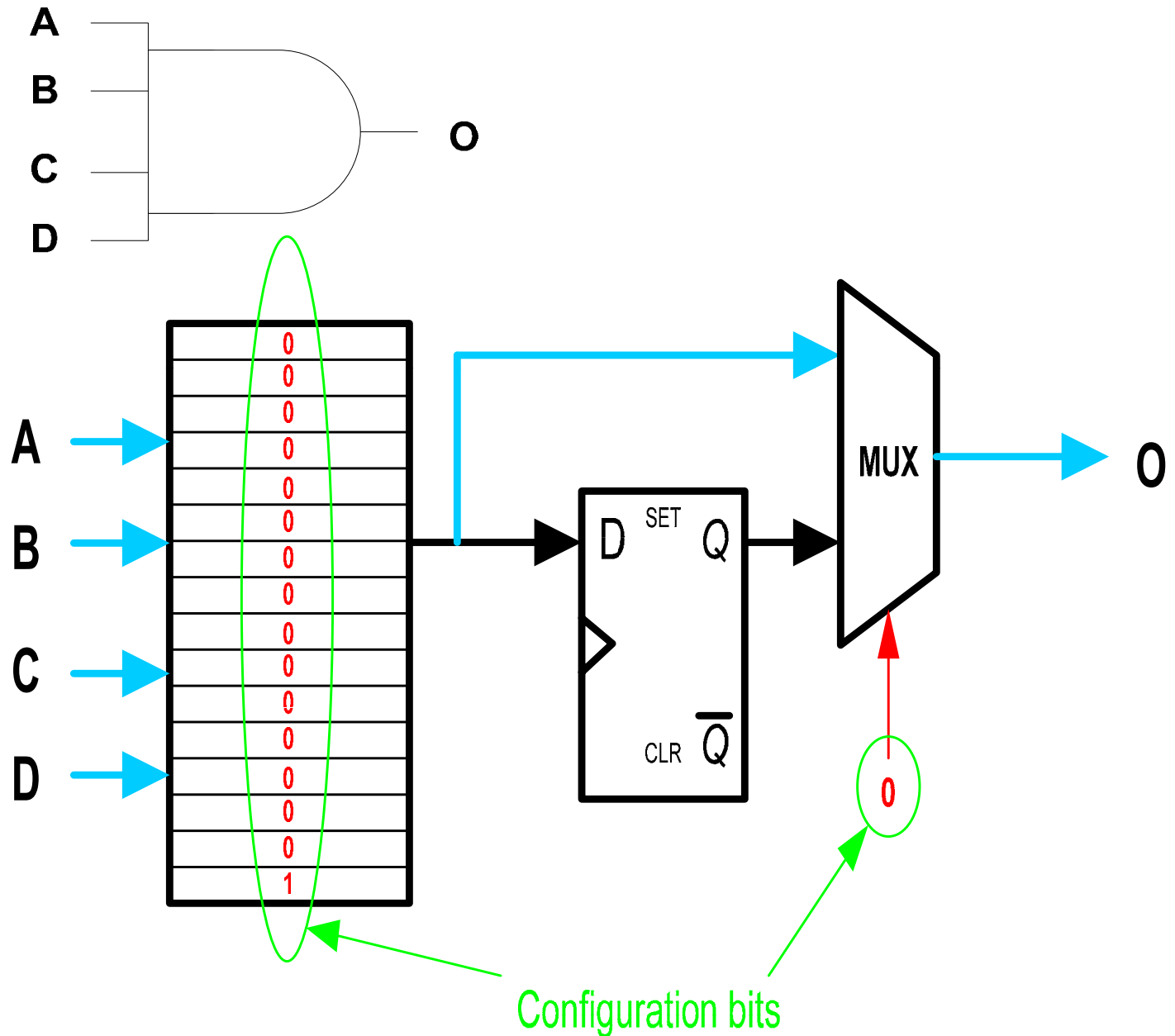


Interconnection Network

 


Configurable Interconnect

 


Placement: Select CLBs

 


Routing: Select path

 

SB1
Configuration bits

 

SB4
Configuration bits

 

Shannon's expansion theorem

Used to implement many variable logic functions using MUX and LUTs

$$f(x_1, x_2, \dots, x_n) = x_1 f(0, x_2, \dots, x_n) + \bar{x}_1 f(1, x_2, \dots, x_n)$$

Since x_1 is a boolean variable, we need to look at only two cases: $x_1 = 0$ and $x_1 = 1$.

- Setting $x_1 = 0$ in the above expression, we have:

$$\begin{aligned} \bullet f(0, x_2, \dots, x_n) &= 1 f(0, x_2, \dots, x_n) + 0 f(1, x_2, \dots, x_n) \\ &= f(0, x_2, \dots, x_n) \end{aligned}$$


- Setting $x_1 = 1$, we have:

$$\begin{aligned} \bullet f(1, x_2, \dots, x_n) &= 0 f(0, x_2, \dots, x_n) + 1 f(1, x_2, \dots, x_n) \\ &= f(1, x_2, \dots, x_n) \end{aligned}$$

FPGA Structures


- Configurable Logic Block (CLB)
 - Two identical slices in each CLB
 - Two LUT in each slice
- CLK - Delay Locked Loop (DLL)

Xilinx Spartan-6 Digilent Atlys Board

 


Special FPGA functions

 - Internal SRAM
- Embedded Multipliers and DSP blocks
- Embedded logic analyzer
- Embedded CPUs
- High speed I/O (~10GHz)
- DDR/DDR2/DDR3 SDRAM interfaces
- PLLs



Comparison

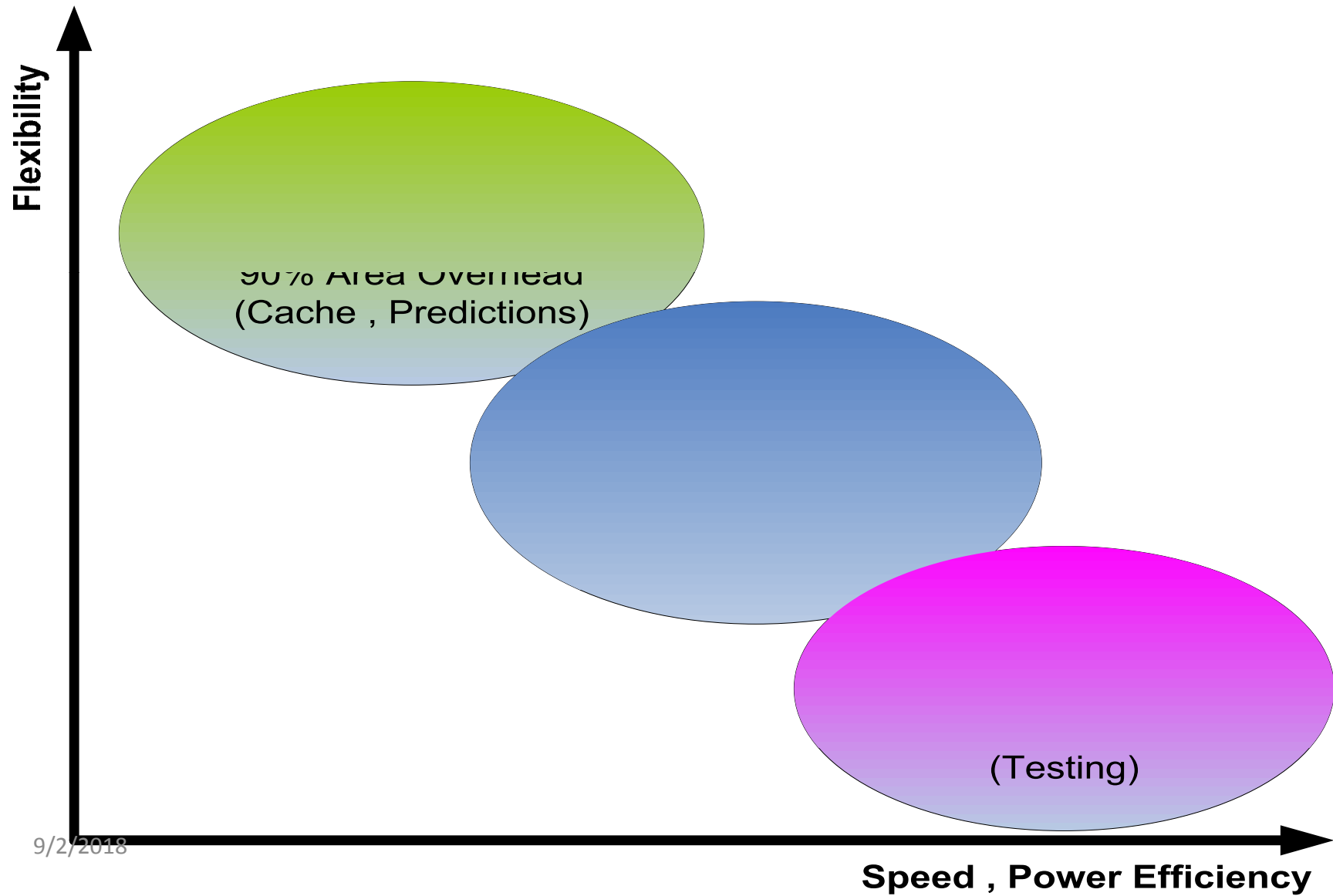

Usages

- Digital designs where ASIC is not commercial
- Reconfigurable systems
- Upgradeable systems
- ASIC prototyping and emulation
- Education

FPGA Manufacturers


- Xilinx
- Altera
- Lattice
- Actel



We will work with Xilinx FPGAs : Next Semester

FPGA and ASIC Design Flow

IC Design Process

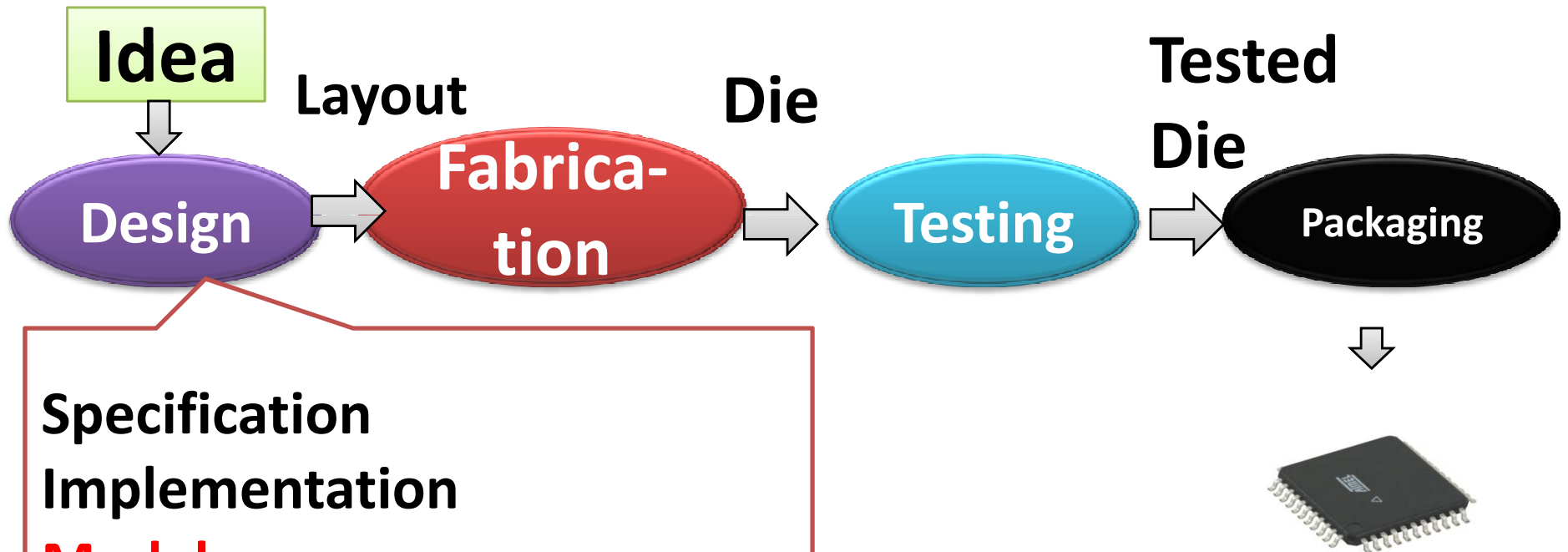

Specification
Implementation
Model
Synthesis
Verification & Simulation

Hardware/Software Design Flow

